



Name: Kerolos Youssef Ghobrial

LAB 1: Linting

Q1.

The major violations that linting tool can detect are:

- Non-Synthesizable constructs
- Unintentional latches
- Unused declarations
- Multiple drivers and undriven signals
- Race conditions
- Incorrect usage of blocking and non-blocking assignments
- Incomplete assignments in subroutines
- Case statement style issues
- Set and reset conflicts
- Out-of-range indexing

Q2.

A-

```
always @ (*)  
a = a & b;
```

Error: combinational loop

Solution: break the loop by a flip-flop as follows:

```
module Q2_a(output reg a, input b,clk,rst);  
  always@(posedge clk,negedge rst)  
  begin  
    if(~rst)  
      a <= 0;
```

```

else
a <= a & b;
end
endmodule

```

B-

```

always @ (posedge clk)
if (a > b)
    c <= a;

```

Error: flip-flop should have an asynchronous set or reset

Solution: put asynchronous reset for flip-flop

```

module Q2_b(output reg c, input a,b,clk,rst);

always@(posedge clk,negedge rst)
begin
if(~rst)
c <= 0;
else if(a > b)
c <= a;
end

endmodule

```

C-

```

always @ (posedge clk)
if (a > b)
c <= a;
c <= b;
else
c <= c;

```

Error: - Do not assign over the same signal in an always construct for sequential circuits

- No begin-end for if statement before else.
- Flip-flop should have an asynchronous set or reset.

Solution: - declare another variable with c variable to assign it to b.

- add begin-end in if statement.
- put asynchronous reset for flip flop

```

module Q2_c(input a,b,clk,rst, output reg c,d);

always@(posedge clk,negedge rst)
begin
if(~rst)
begin
c <= 0;
d <= 0;
end

else if (a > b)
begin
c <= a;
d <= b;
end

else
c <= c;

end

endmodule

```

D-

```

wire [3:0] a;
wire [7:0] b;
assign a = b;

```

Error: - LHS width is less than RHS width of assignment
- Block should not contain feedthroughs.

Solution: - make size of LHS equal to size of RHS and solve feedthroughs using buffer.

```

module Q2_d(
input [7:0] b,
output [7:0] a
);
buf b1(a,b);

endmodule

```

E-

```

input A;
input B;
output C;

assign C = A;

```

Error: An input has been declared but not read

Solution: remove input B.

```
module Q2_e(  
  input a,  
  output c);  
  
  assign c = a;  
endmodule
```

F-

```
A = 32'bx;
```

Error: - RHS of the assignment contains X.

- Based number 32'bx has no meaning in synthesis.

Solution: - assign another value for A

```
module Q2_f(  
  output [31:0] A  
);  
  assign A = 32'b1;  
endmodule
```

G-

```
reg [1:0] v;  
case (v)  
  00: x = 1  
  10: x = 0  
endcase
```

Error: - case statement(or selected signal assignment) does not have a default or OTHERS clause.

- Latch inferred for signal 'x' in module 'Q2_g'.

Solution: - add default statement

```
module Q2_g(  
  input [1:0] v,  
  output reg x  
);  
  always @(*) begin  
    case(v)  
      2'b00: x = 1'b1;  
      2'b10: x = 1'b0;  
      default: x = 1'b1;  
    endcase  
  end
```

```
end  
endmodule
```

H-

```
assign out = en ? in : out;  
or  
assign a = en ? z : c;  
assign z = en ? a : y;
```

Error: - Combinational loop exists at 'Q2_h.a- Q2_h.z- Q2_h.out'.



- Reserved name 'out'.

Solution: - change in assign statements to eliminate combinational loops

```
module Q2_h(  
  input wire en,inp,c,y,  
  output wire out,a,z  
);  
assign out = en? inp:c;  
  
assign a = en? y:c;  
assign z = en? inp:y;  
endmodule
```

I-
 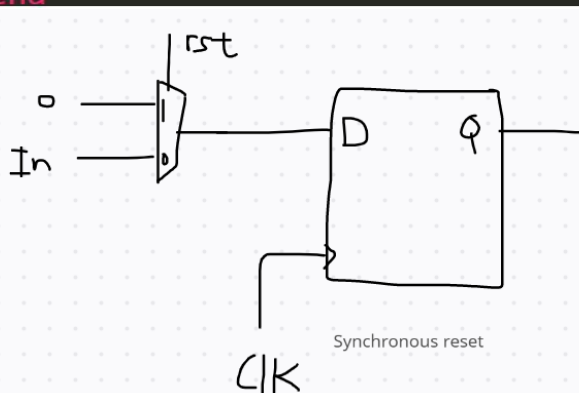
```
always @(posedge clk or posedge rst)  
begin  
  if(rst)  
    out1 <= 0;  
  else  
    out1 <= in;  
  end  
always@(posedge clk)  
begin  
  if(rst)  
    out2 <= 0;  
  else  
    out2 <= in;  
  end  
end
```



Error: - Flip-flop 'out2' has neither asynchronous set nor asynchronous reset.

- Asynchronous reset signal 'lint.rst' (flop: 'Q2_i.out1') used as non reset/synchronous-reset at instance 'Q2_i.out2_reg.D'

Solution: - put asynchronous reset for flip flop of out2

```
module Q2_i (  
  input wire clk,rst,in,  
  output reg out1,out2  
);  
always @(posedge clk or posedge rst) begin  
  
  if(rst) begin  
    out1 <= 1'b0;  
  end  
  else begin  
    out1 <= in;  
  end  
end  
  
always @(posedge clk or posedge rst) begin  
  if(rst) begin  
    out2 <= 1'b0;  
  end  
  else begin  
    out2 <= in;  
  end  
end  
endmodule
```